

Computer system architecture

Chapt 4. Register transfer & Microoperations

KyuheonKim@khu.ac.kr

Rm: 416

REGISTER TRANSFER AND MICROOPERATIONS

- Register Transfer Language
- Register Transfer
- Bus and Memory Transfers
- Arithmetic Microoperations
- Logic Microoperations
- Shift Microoperations
- Arithmetic Logic Shift Unit

SIMPLE DIGITAL SYSTEMS


- ❖ **Combinational and sequential circuits (learned in Chapters 1 and 2) can be used to create simple digital systems.**
- ❖ **These are the low-level building blocks of a digital computer.**
- ❖ **Simple digital systems are frequently characterized in terms of**
 - ◆ **the registers they contain, and**
 - ◆ **the operations that they perform.**
 - ◆ **the control that initiates the sequence of microoperations**
- ❖ **Typically,**
 - ◆ **What operations are performed on the data in the registers**
 - ◆ **What information is passed between registers**

MI CROOPERATI ONS (1)

- ❖ **The operations on the data in registers are called microoperations.**
- ❖ **The functions built into registers are examples of microoperations**
 - ◆ **Shift**
 - ◆ **Load**
 - ◆ **Clear**
 - ◆ **Increment**
 - ◆ **...**

MI CROOPERATI ON (2)

 An elementary operation performed (during one clock pulse), on the information stored in one or more registers



$$R \leftarrow f(R, R)$$

f: shift, load, clear, increment, add, subtract, complement, and, or, xor, ...

REGISTER TRANSFER LANGUAGE

- ❖ Rather than specifying a digital system in words, a specific notation is used, *register transfer language*

- ❖ For any function of the computer, the register transfer language can be used to describe the (sequence of) microoperations

- ❖ Register transfer language
 - ◆ A symbolic language
 - ◆ A convenient tool for describing the internal organization of digital computers
 - ◆ Can also be used to facilitate the design process of digital systems.

DESIGNATION OF REGISTERS

- ❖ Registers are designated by capital letters, sometimes followed by numbers (e.g., A, R13, IR)
- ❖ Often the names indicate function:
 - ◆ MAR - memory address register
 - ◆ PC - program counter
 - ◆ IR - instruction register
- ❖ Registers and their contents can be viewed and represented in *various ways*
 - ◆ A register can be viewed as a single entity:




- ◆ Registers may also be represented showing the bits of data they contain

DESIGNATION OF REGISTERS

- Designation of a register
 - a register
 - portion of a register
 - a bit of a register


- Common ways of drawing the block diagram of a register

Register

 

Numbering of bits

Showing individual bits

 

Subfields

REGISTER TRANSFER

- ❖ Copying the contents of one register to another is a register transfer
- ❖ A register transfer is indicated as

$R2 \leftarrow R1$

- ◆ In this case the contents of register R2 are copied (loaded) from register R1
- ◆ A simultaneous transfer of all bits from the source R1 to the destination register R2, during one clock pulse
- ◆ Note that this is a non-destructive; i.e. the contents of R1 are not altered by copying (loading) them to R2

REGISTER TRANSFER

❖ A register transfer such as

$R3 \leftarrow R5$

Implies that the digital system has

- ◆ the data lines from the source register (R5) to the destination register (R3)
- ◆ Parallel load in the destination register (R3)
- ◆ Control lines to perform the action

CONTROL FUNCTIONS

- ❖ Often actions need to only occur if a certain condition is true
- ❖ This is similar to an “if” statement in a programming language
- ❖ In digital systems, this is often done via a *control signal*, called a *control function*
 - ◆ If the signal is 1, the action takes place
- ❖ This is represented as:

P: $R2 \leftarrow R1$


Which means “if $P = 1$, then load the contents of register R1 into register R2”, i.e., if $(P = 1)$ then $(R2 \leftarrow R1)$

HARDWARE IMPLEMENTATION OF CONTROLLED TRANSFERS


Implementation of controlled transfer

P: $R2 \leftarrow R1$

Block diagram

 

Timing diagram

 

- The same clock controls the circuits that generate the control function and the destination register
- Registers are assumed to use *positive-edge-triggered* flip-flops

SI MULTANEIOUS OPERATI ONS

- ❖ If two or more operations are to occur simultaneously, they are separated with commas

P: R3 ← R5, MAR ← I R

- ❖ Here, if the control function $P = 1$, load the contents of R5 into R3, and at the same time (clock), load the contents of register I R into register MAR

BASIC SYMBOLS FOR REGISTER TRANSFERS

Symbols	Description	Examples
Capital letters & numerals	Denotes a register	MAR, R2
Parentheses ()	Denotes a part of a register	R2(0-7), R2(L)
Arrow ←	Denotes transfer of information	R2 ← R1
Colon :	Denotes termination of control function	P:
Comma ,	Separates two micro-operations	A ← B, B ← A



CONNECTING REGISTERS

- ❖ In a digital system with many registers, it is impractical to have data and control lines to directly allow each register to be loaded with the contents of every possible other registers
- ❖ To completely connect n registers $\rightarrow n(n-1)$ lines
- ❖ $O(n^2)$ cost
 - ◆ This is not a realistic approach to use in a large digital system
- ❖ Instead, take a different approach
- ❖ Have one centralized set of circuits for data transfer – the bus
- ❖ Have control circuits to select which register is the source, and which is the destination


BUS AND BUS TRANSFER

Bus is a path (of a group of wires) over which information is transferred, from any of several sources to any of several destinations.

 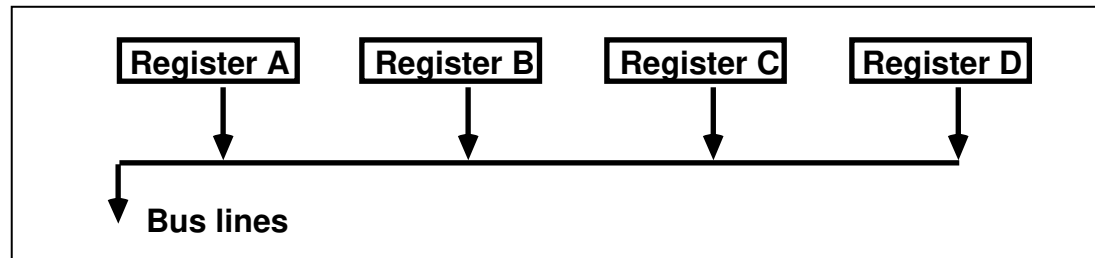From a register to bus: $BUS \leftarrow R$




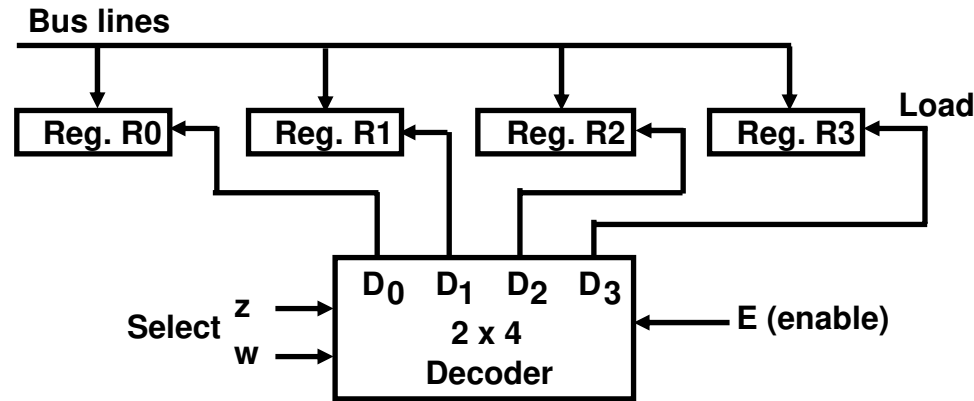TRANSFER FROM BUS TO A DESTINATION REGISTER




Three-State Bus Buffers

Normal input A
Control input C

 

Output $Y=A$ if $C=1$
High-impedance if $C=0$

Bus line with three-state buffers

 

BUS TRANSFER IN RTL

- ❖ Depending on whether the bus is to be mentioned explicitly or not, register transfer can be indicated as either

$R2 \leftarrow R1$


or

$BUS \leftarrow R1, R2 \leftarrow BUS$

- ❖ In the former case the bus is implicit, but in the latter, it is explicitly indicated


MEMORY (RAM)

- ❖ Memory (RAM) can be thought as a sequential circuits containing some number of registers
- ❖ These registers hold the *words* of memory
- ❖ Each of the r registers is indicated by an *address*
- ❖ These addresses range from 0 to $r-1$
- ❖ Each register (word) can hold n bits of data
- ❖ Assume the RAM contains $r = 2^k$ words. It needs the following
 - ◆ n data input lines
 - ◆ n data output lines
 - ◆ k address lines
 - ◆ A Read control line
 - ◆ A Write control line

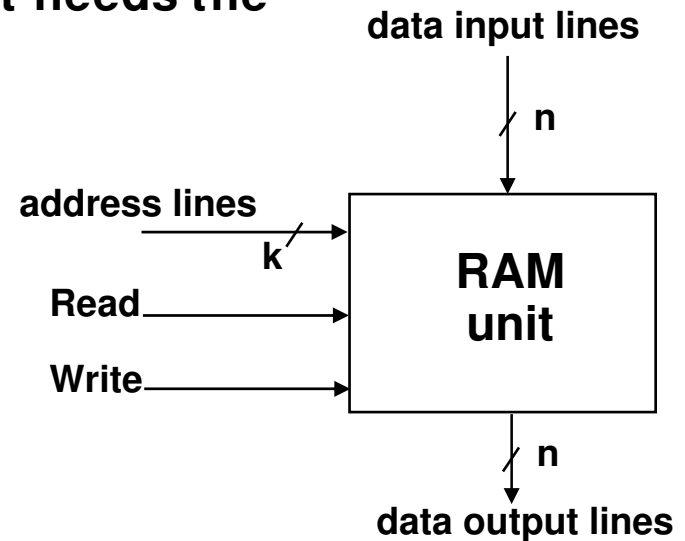

MEMORY TRANSFER

- ❖ Collectively, the memory is viewed at the register level as a device, **M**.
- ❖ Since it contains multiple locations, we must specify which address in memory we will be using
- ❖ This is done by indexing memory references
- ❖ Memory is usually accessed in computer systems by putting the desired address in a special register, the *Memory Address Register (MAR, or AR)*
- ❖ When memory is accessed, the contents of the MAR get sent to the memory unit's address lines

 

MEMORY READ

- ❖ To read a value from a location in memory and load it into a register, the register transfer language notation looks like this:

$$R1 \leftarrow M[MAR]$$

- ❖ This causes the following to occur
 - ◆ The contents of the MAR get sent to the memory address lines
 - ◆ A Read (= 1) gets sent to the memory unit
 - ◆ The contents of the specified address are put on the memory's output data lines
 - ◆ These get sent over the bus to be loaded into register R1

MEMORY WRITE

- ❖ To write a value from a register to a location in memory looks like this in register transfer language:

$$M[MAR] \leftarrow R1$$

- ❖ This causes the following to occur
 - ◆ The contents of the MAR get sent to the memory address lines
 - ◆ A Write (= 1) gets sent to the memory unit
 - ◆ The values in register R1 get sent over the bus to the data input lines of the memory
 - ◆ The values get loaded into the specified address in the memory

SUMMARY OF R. TRANSFER MICROOPERATIONS

$A \leftarrow B$

Transfer content of reg. B into reg. A

$AR \leftarrow DR(AD)$

Transfer content of AD portion of reg. DR into reg. AR

$A \leftarrow \text{constant}$

Transfer a binary constant into reg. A

$ABUS \leftarrow R1,$

Transfer content of R1 into bus A and, at the same time,

$R2 \leftarrow ABUS$

transfer content of bus A into R2

AR

Address register

DR

Data register

$M[R]$

Memory word specified by reg. R

M

Equivalent to $M[AR]$

$DR \leftarrow M$

Memory *read* operation: transfers content of memory word specified by AR into DR

$M \leftarrow DR$

Memory *write* operation: transfers content of DR into memory word specified by AR

MI CROOPERATI ONS

- **Computer system microoperations are of four types:**
 - **Register transfer microoperations**
 - **Arithmetic microoperations**
 - **Logic microoperations**
 - **Shift microoperations**

ARITHMETIC MICROOPERATIONS

- ❖ The basic arithmetic microoperations are
 - ◆ Addition
 - ◆ Subtraction
 - ◆ Increment
 - ◆ Decrement


- ❖ The additional arithmetic microoperations are
 - ◆ Add with carry
 - ◆ Subtract with borrow
 - ◆ Transfer/ Load
 - ◆ etc. ...

Summary of Typical Arithmetic Micro-Operations


$R3 \leftarrow R1 + R2$	Contents of R1 plus R2 transferred to R3
$R3 \leftarrow R1 - R2$	Contents of R1 minus R2 transferred to R3
$R2 \leftarrow R2'$	Complement the contents of R2
$R2 \leftarrow R2' + 1$	2's complement the contents of R2 (negate)
$R3 \leftarrow R1 + R2' + 1$	subtraction
$R1 \leftarrow R1 + 1$	Increment
$R1 \leftarrow R1 - 1$	Decrement

BINARY ADDER / SUBTRACTOR / INCREMENTER


Binary Adder

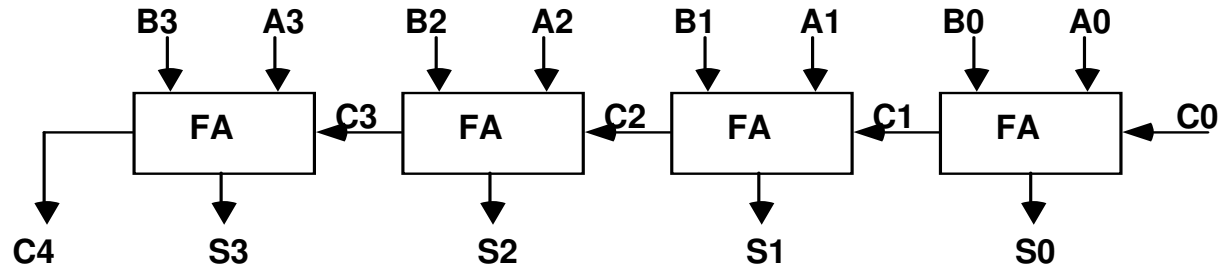


Binary Adder-Subtractor

 

Binary Incrementer

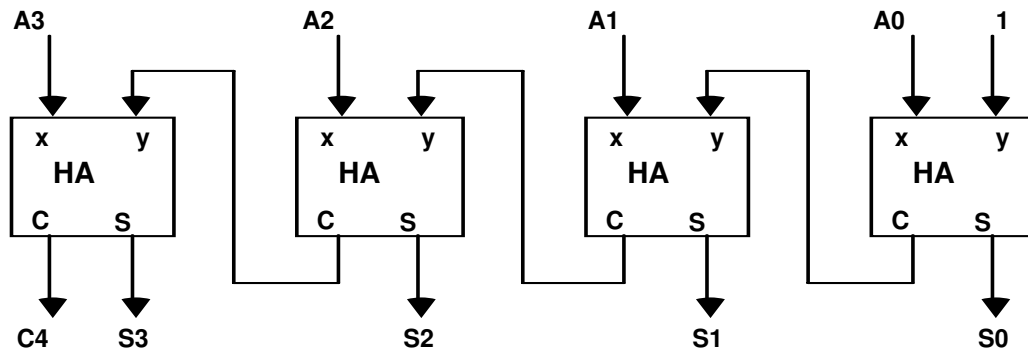


ARITHMETIC CIRCUIT

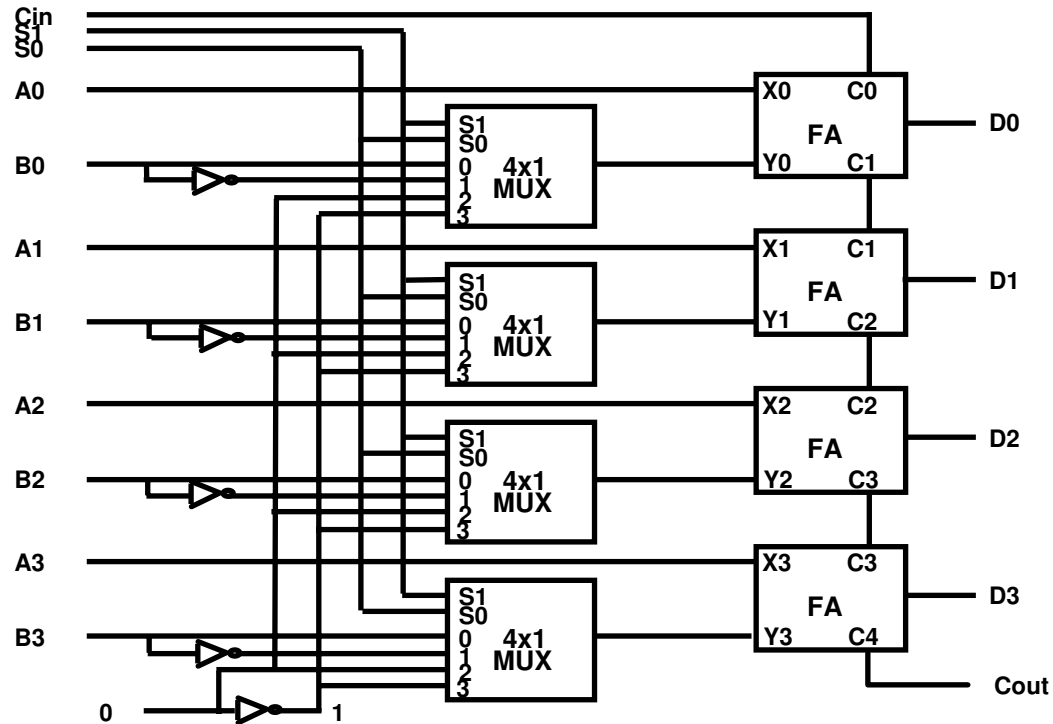

S1	S0	Cin	Y	Output	Microoperation
0	0	0	B	$D = A + B$	Add
0	0	1	B	$D = A + B + 1$	Add with carry
0	1	0	B'	$D = A + B'$	Subtract with borrow
0	1	1	B'	$D = A + B' + 1$	Subtract
1	0	0	0	$D = A$	Transfer A
1	0	1	0	$D = A + 1$	Increment A
1	1	0	1	$D = A - 1$	Decrement A
1	1	1	1	$D = A$	Transfer A

LOGIC MICROOPERATIONS

 


Function table

S_1	S_0	Output	μ -operation
0	0	$F = A \wedge B$	AND
0	1	$F = A \vee B$	OR
1	0	$F = A \oplus B$	XOR
1	1	$F = A'$	Complement


SHIFT MICROOPERATIONS

- ❖ There are three types of shifts
 - ◆ *Logical shift*
 - ◆ *Circular shift*
 - ◆ *Arithmetic shift*
- ❖ What differentiates them is the information that goes into the serial input

- A right shift operation

 


- A left shift operation

 


LOGICAL SHIFT

❖ In a logical shift the serial input to the shift is a 0.

❖ A right logical shift operation:

 

❖ A left logical shift operation:

 

❖ In a Register Transfer Language, the following notation is used

- ◆ *shl* for a logical shift left
- ◆ *shr* for a logical shift right
- ◆ Examples:


✓ $R2 \leftarrow shr R2$

✓ $R3 \leftarrow shl R3$


CIRCULAR SHIFT

- ❖ In a circular shift the serial input is the bit that is shifted out of the other end of the register.

- ❖ A right circular shift operation:

 

- ❖ A left circular shift operation:

 

- ❖ In a RTL, the following notation is used


- ◆ *cil* for a circular shift left
- ◆ *cir* for a circular shift right

- ◆ Examples:


- ✓ $R2 \leftarrow cir R2$
- ✓ $R3 \leftarrow cil R3$

ARITHMETIC SHIFT

 - ❖ An arithmetic shift is meant for signed binary numbers (integer)
- ❖ An arithmetic left shift multiplies a signed number by two
- ❖ An arithmetic right shift divides a signed number by two
- ❖ The main distinction of an arithmetic shift is that it must keep the sign of the number the same as it performs the multiplication or division
- ❖ A right arithmetic shift operation:




- ❖ A left arithmetic shift operation:

 


ARITHMETIC SHIFT

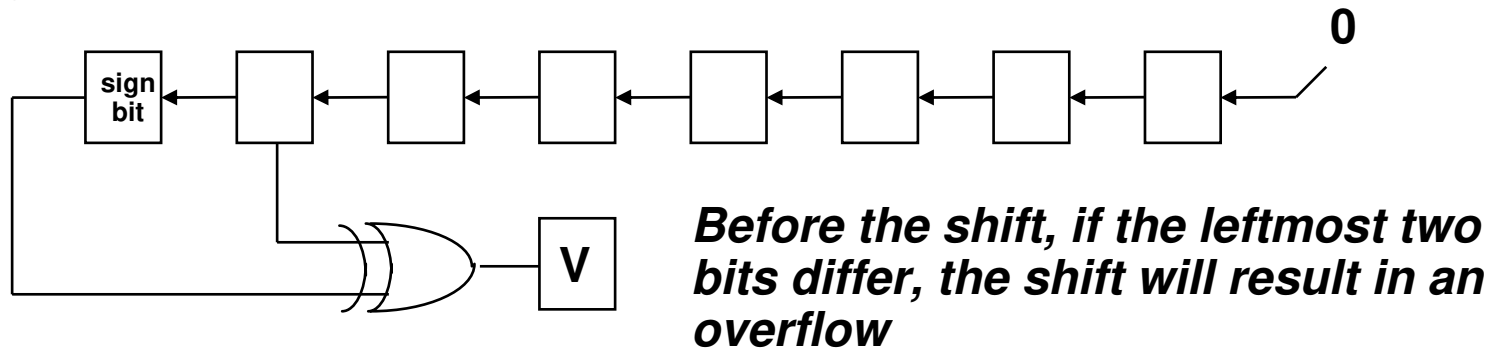- ❖ An left arithmetic shift operation must be checked for the overflow




- ❖ In a RTL, the following notation is used
 - ◆ *ashl* for an arithmetic shift left
 - ◆ *ashr* for an arithmetic shift right
 - ◆ Examples:
 - ✓ $R2 \leftarrow ashr R2$
 - ✓ $R3 \leftarrow ashl R3$

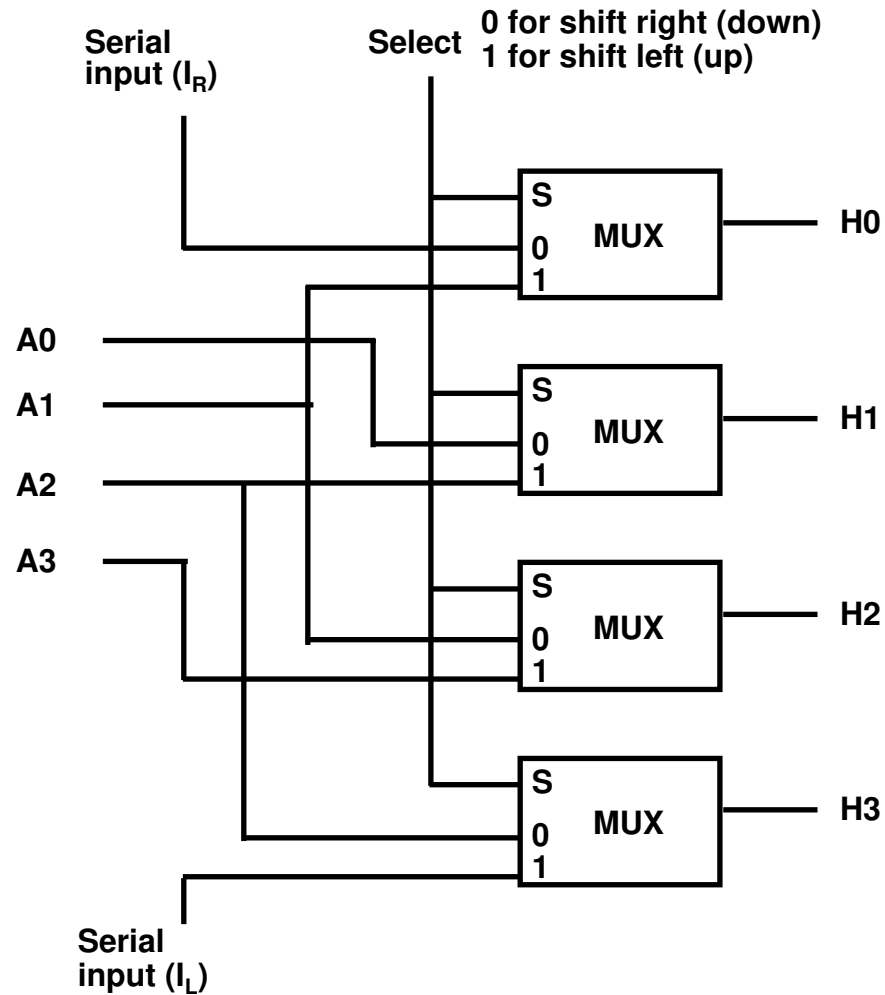HARDWARE IMPLEMENTATION OF SHIFT MICROOPERATIONS



ARITHMETIC LOGIC SHIFT UNIT

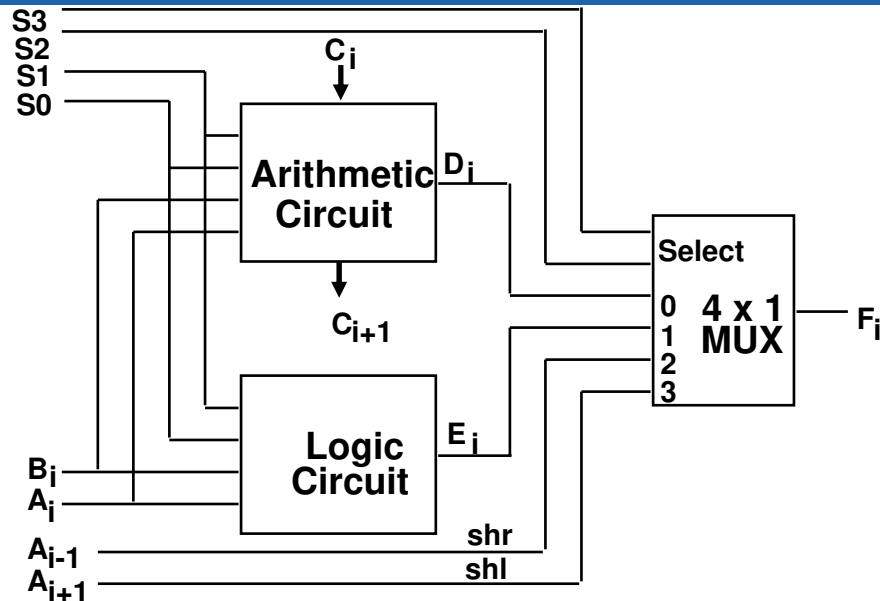

S3	S2	S1	S0	Cin	Operation	Function
0	0	0	0	0	$F = A$	Transfer A
0	0	0	0	1	$F = A + 1$	Increment A
0	0	0	1	0	$F = A + B$	Addition
0	0	0	1	1	$F = A + B + 1$	Add with carry
0	0	1	0	0	$F = A + B'$	Subtract with borrow
0	0	1	0	1	$F = A + B' + 1$	Subtraction
0	0	1	1	0	$F = A - 1$	Decrement A
0	0	1	1	1	$F = A$	Transfer A
0	1	0	0	X	$F = A \wedge B$	AND
0	1	0	1	X	$F = A \vee B$	OR
0	1	1	0	X	$F = A \oplus B$	XOR
0	1	1	1	X	$F = A'$	Complement A
1	0	X	X	X	$F = shr A$	Shift right A into F
1	1	X	X	X	$F = shl A$	Shift left A into F